
Lösningsförslag övningsuppgifter 2023-04-06


- 1. Genomför följande aritmetiska operationer på 4-bitars binär form:
 - a) 5 + 7
 - b) 15 5
 - c) 5 * 3
 - d) 15/5

Lösningsförslag:


Binära operationer kan genomföras på samma sätt som för decimala tal. I detta fall används liggande stolen för division.

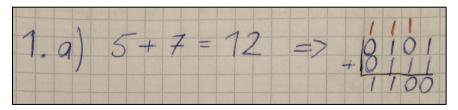


Figur 1: Binär addition.

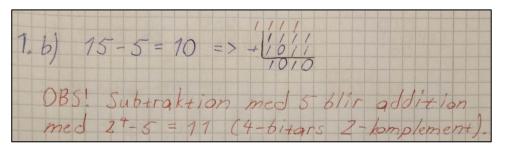

Figur 2: Binär subtraktion med 4-bitars 2-komplement.

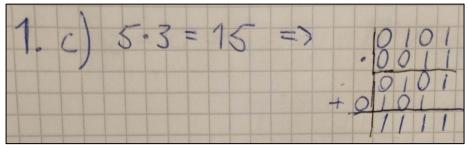

Figur 3: Binär multiplikation.

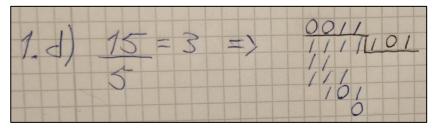

Figur 4: Binär division med liggande stolen.

Division med liggande stolen sker från vänster till höger, där kvot q samt rest r beräknas:

- $1 < 101 \Rightarrow q_3 = 0$, lägg till biten till höger \Rightarrow division med 11 i stället för 1
- $11 < 101 \Rightarrow q_2 = 0$, lägg till biten till höger \Rightarrow division med 111 i stället för 11
- $111/101 = 7/5 \Rightarrow q_1 = 1$, $r_0 = 10 \Rightarrow lagg till biten till höger <math>\Rightarrow n$ nästa gång division med 101
- $101/101 = 5/5 \Rightarrow q_0 = 1$, $r_0 = 0 \Rightarrow lnga fler bitar till höger, beräkningen är klar$

Därmed gäller att kvoten $q = 0011 \Rightarrow 15 / 3 = 1111 / 101 = 0011$.

Hårdvarunära programmering

2. Rita upp en OR-grind med CMOS-transistorer och visa spänningsfallen i kretsen för samtliga kombinationer 00 – 11 av insignaler A och B.

Lösningsförslag:


För en OR-grind gäller att

- X = 1 om A = 1 eller B = 1, vilket skrivs som X = A + B.
- X = 0 om A = 0 och B = 0, vilket skrivs som X' = A' * B'.

Det nedre och övre nätet ska ha motsatt funktion, så att endast en av delarna leder vid ett givet tillfälle. Vi kopplar det nedre nätet som X = A + B och det övre nätet som X' = A' * B' och får då en NOR-grind (då transistorswitchar inverterar naturligt när de leder. Sedan kopplas en NOT-grind på NOR-grindens utgång för att realisera OR-grinden.

Se figuren nedan. Notera att signal X = U', dvs. inversen till U:

- Koppla det nedre nätet som X = A + B => parallella transistorer med A och B som insignaler. För att det nedre nätet ska leda måste då antingen A eller B vara 1. Då blir signalen U = 0 och därmed X = 1.
- Koppla det övre nätet som X' = A' * B' => seriella transistorer med A och B som insignaler (A' respektive B' kan läsas som att av respektive B måste vara 0 för att ansluten transistor ska leda). För att det övre nätet ska leda måste då både A och B vara 0. Då blir signalen U = 1 och därmed X = 0.
- Vi har nu skapat en NOR-grind. Vi ansluter en NOT-grind till utgången och realiserar då en OR-grind.

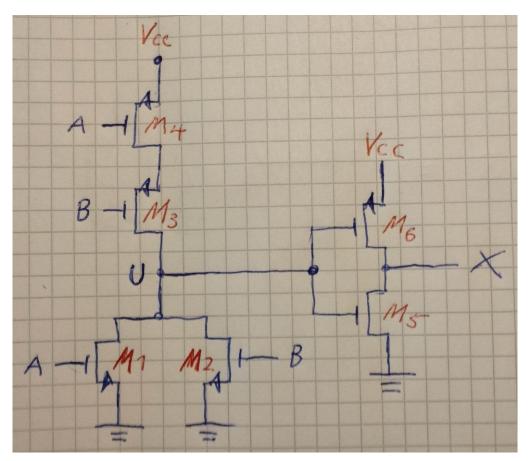

Figur 5: OR-grind realiserad med CMOS-transistorer.

Hårdvarunära programmering

3. Förklara skillnaden mellan deklaration av ett package samt en package body i VHDL.

Lösningsförslag:

Ett package består av en header (kallad package) samt en kropp (kallad package body):

- Package innehåller deklaration av konstanter, typer, submoduler och komponenter.
- Package body innehåller definition av submoduler (funktioner och procedurer).

Som exempel, se package misc i bilaga A.

4. Definiera en funktion i VHDL som indikerar ifall ett givet tal *number* är jämnt eller inte genom att returnera *true* eller *false*. Talet i fråga ska tillhöra datatypen *natural*.

Lösningsförslag:

```
-- number_is_even: Indicates if specified number is even.
-- - number: The number to check.
-- - return: True if the number is even, else false.

function number_is_even(constant number: natural)
return boolean is
constant bits: std_logic_vector(31 downto 0) := std_logic_vector(to_unsigned(number, 32));
begin
    if (bits(0) = '0') then
        return true;
    else
        return false;
    end if;
end function;
```

3

Bilaga A – Filen misc.vhd innehållande package misc

```
-- misc.vhd: Contains miscellaneous functions and constants via package misc.
______
library ieee;
use ieee.std logic 1164.all;
use ieee.numeric_std.all;
package misc is
______
-- Binary codes for hexadecimal digits 0x00 - 0x0F:
constant OFF : std_logic_vector(6 downto 0) := "11111111";
constant ZERO : std_logic_vector(6 downto 0) := "10000000"
constant ONE : std_logic_vector(6 downto 0) := "1111001";
constant TWO : std_logic_vector(6 downto 0) := "0100100";
constant THREE: std_logic_vector(6 downto 0) := "0110000";
constant FOUR : std_logic_vector(6 downto 0) := "0011001";
constant FIVE : std_logic_vector(6 downto 0) := "0010010";
constant SIX : std_logic_vector(6 downto 0) := "0000010";
constant SEVEN: std_logic_vector(6 downto 0) := "1111000";
constant EIGHT: std_logic_vector(6 downto 0) := "0000000";
constant NINE : std_logic_vector(6 downto 0) := "0010000";
constant A : std_logic_vector(6 downto 0) := "0001000";
constant B : std logic vector(6 downto 0) := "0000011";
constant C : std_logic_vector(6 downto 0) := "1000110";
constant D : std_logic_vector(6 downto 0) := "0100001";
          : std_logic_vector(6 downto 0) := "0000110";
constant E
constant F : std_logic_vector(6 downto 0) := "0001110";
-- to_natural: Converts a std_logic_vector to a natural (unsigned) number.
--
              - vector: The vector whose content is to be converted.
             - return: Corresponding natural number.
function to natural(constant vector: std logic vector)
return natural;
-- to_std_logic_vector: Converts a natural (unsigned) number to std_logic_vector.
                      - number : The number to be converted.
                      - vector size: The size (number of bits) of the
                                    returned vector (default = 32).
                      - return: Corresponding std_logic_vector (i.e. bits).
function to_std_logic_vector(constant number : natural;
                          constant vector_size: natural := 32)
return std_logic_vector;
-- add: Adds specified numbers and returns the sum as std logic vector.
                  : Vector containing the first number.
       - X
       - y : Vector containing the second number.
       - vector size: The size of the returned vector (default = 32).
_ _
       - return: The sum of the numbers as std logic vector.
-----
function add(constant x, y : std_logic_vector;
           constant vector_size: natural := 32)
return std_logic_vector;
```

```
-- subtract: Subtracts specified numbers with 2-complement and returns the
           difference as std_logic_vector.
--
            - x- y: Vector containing the first number.- y: Vector containing the second number.
            - vector_size: The size of the returned vector (default = 32).
--
            - return: The difference between the numbers as std_logic_vector.
function subtract(constant x, y : std_logic_vector;
                constant vector_size: natural := 32)
return std_logic_vector;
______
-- get_binary_code: Returns the binary code of specified hexadecimal digit.
                   - digit: Hexadecimal digit whose binary code is returned.
                  - return: The binary code of specified digit.
______
function get_binary_code(constant digit: std_logic_vector(3 downto 0))
return std_logic_vector;
end package;
package body misc is
-- to natural: Converts a std logic vector to a natural (unsigned) number.
             - vector: The vector whose content is to be converted.
             - return: Corresponding natural number.
function to_natural(constant vector: std_logic_vector)
return natural is
begin
   return to integer(unsigned(vector));
end function;
-- to std logic vector: Converts a natural (unsigned) number to std logic vector.
                      - number : The number to be converted.
                      - vector_size: The size (number of bits) of the
___
                                    returned vector (default = 32).
                      return: Corresponding std_logic_vector (i.e. bits).
function to_std_logic_vector(constant number : natural;
                           constant vector_size: natural := 32)
\textbf{return} \ \texttt{std\_logic\_vector} \ \textbf{is}
   return std_logic_vector(to_unsigned(number, vector_size));
end function;
```

```
-- add: Adds specified numbers and returns the sum as std_logic_vector.
       - x
                    : Vector containing the first number.
        - y
                    : Vector containing the second number.
        - vector size: The size of the returned vector (default = 32).
       - return: The sum of the numbers as std_logic_vector.
function add(constant x, y : std logic vector;
       constant vector_size: natural := 32)
return std_logic_vector is
constant sum: natural := to natural(x) + to natural(y);
  return to_std_logic_vector(sum, vector_size);
end function;
-- subtract: Subtracts specified numbers with 2-complement and returns the
            difference as std_logic_vector.
             - x- y: Vector containing the first number.- y: Vector containing the second number.
___
             - vector_size: The size of the returned vector (default = 32).
             - return: The difference between the numbers as std logic vector.
function subtract(constant x, y : std_logic_vector;
                  constant vector_size: natural := 32)
return std_logic_vector is
constant difference: natural := to_natural(x) + (2 ** vector_size - to_natural(y));
  return to_std_logic_vector(difference, vector_size);
end function;
-- get_binary_code: Returns the binary code of specified hexadecimal digit.
___
                    - digit: Hexadecimal digit whose binary code is returned.
--
                    - return: The binary code of specified digit.
function get binary code(constant digit: std logic vector(3 downto 0))
return std logic vector is
begin
    case (digit) is
        when "0000" => return ZERO;
        when "0001" => return ONE;
        when "0010" => return TWO;
        when "0011" => return THREE;
        when "0100" => return FOUR;
        when "0101" => return FIVE;
        when "0110" => return SIX;
        when "0111" => return SEVEN;
        when "1000" => return EIGHT;
        when "1001" => return NINE;
        when "1010" => return A;
        when "1011" => return B;
when "1100" => return C;
when "1101" => return D;
        when "1110" => return E;
        when "1111" => return F;
        when others => return OFF;
    end case;
end function;
end package body;
```